


Intel and Advanced Micro Devices (AMD) both sell compatible microprocessors conforming to the x86 architecture. Intel Pentium III and Pentium 4 microprocessors were largely advertised according to clock frequency in the late 1990s and early 2000s, because Intel offered higher clock frequencies than its competitors. However, Intel's main competitor, AMD, sold Athlon microprocessors that executed programs faster than Intel's chips at the same clock frequency. Why?

- instructions/clock cycle
- frequency not the only factor; lower clock frequency but better performing
- Zen, Zen 2 - AMD microarchitectures that implement x86 architecture

MULTI-CYCLE PROCESSOR

- Processor: datapath (functional blocks), control (control signals)
 - ↓ where data flows
 - ↓ manipulates data
- Register file + ALU

ALU - Arithmetic and Logic Unit

 

ALUControl[2:0]

$F_{2:0}$	Function
000	A & B AND
001	A B OR
010	A + B add
011	not used
100	A & ~B
101	A ~B
110	A - B sub
111	SLT shift left


8 functions:
3 inputs

Architectural State

- PC
- Registers
- Memory

3 components

→ outside microprocessor; external

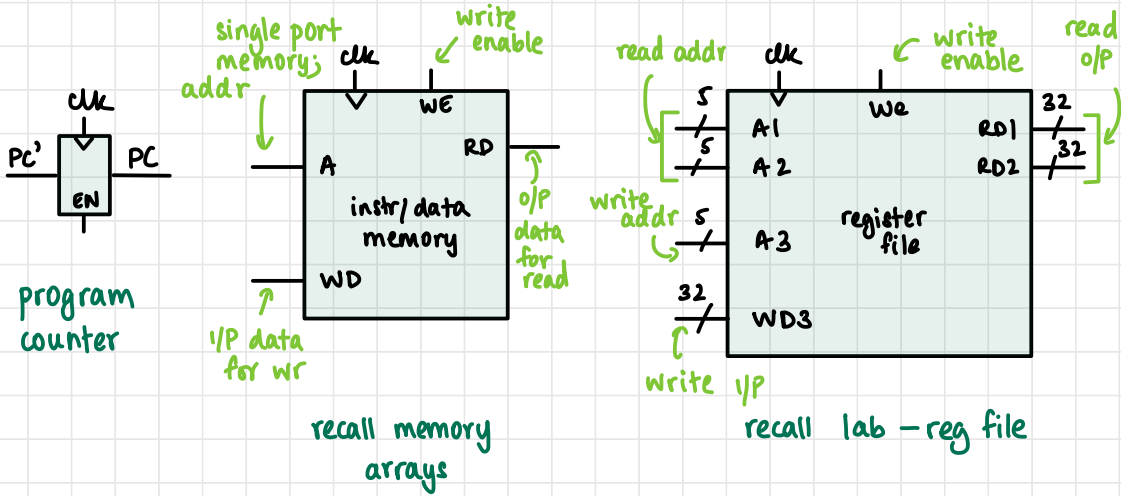


Load Word Instruction


Lw $\$s0, 5(\$t1)$ → load from memory
 rt rs

- Address calculation
 base address ($\$t1$) + offset (5)

Step 0 - Fetch Instruction

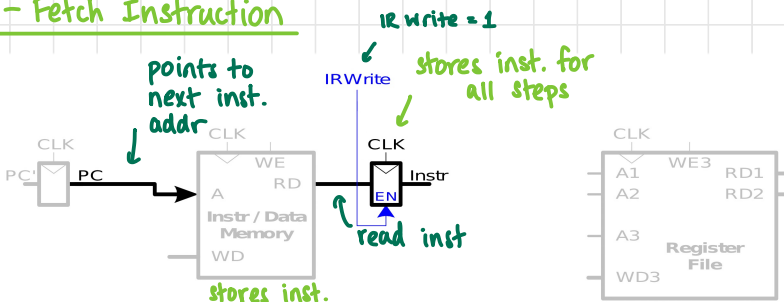


Step 1 - Read source operands from RF

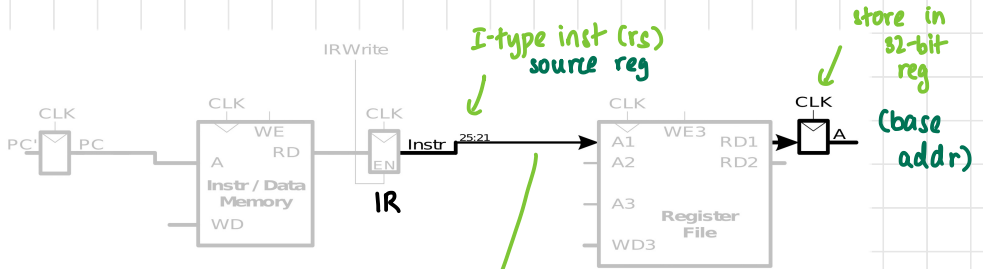

Recall: I-type instruction



 
Step 2 - Read & Sign Extend the Immediate




Recall: I-type instruction




Step 3 - Compute Memory Address

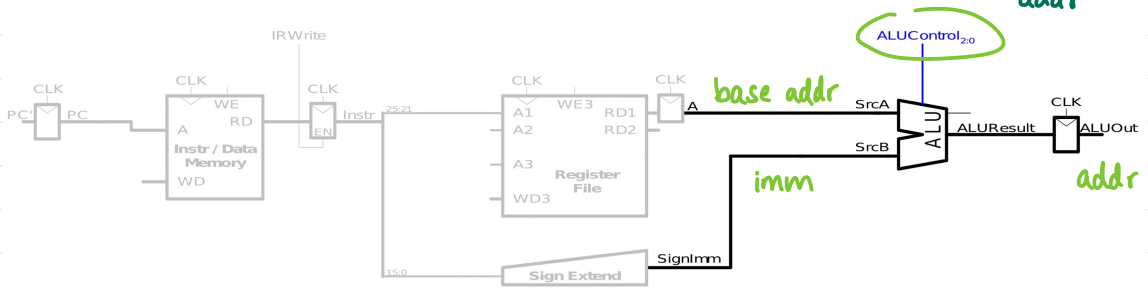

Step 4 - Read from Memory

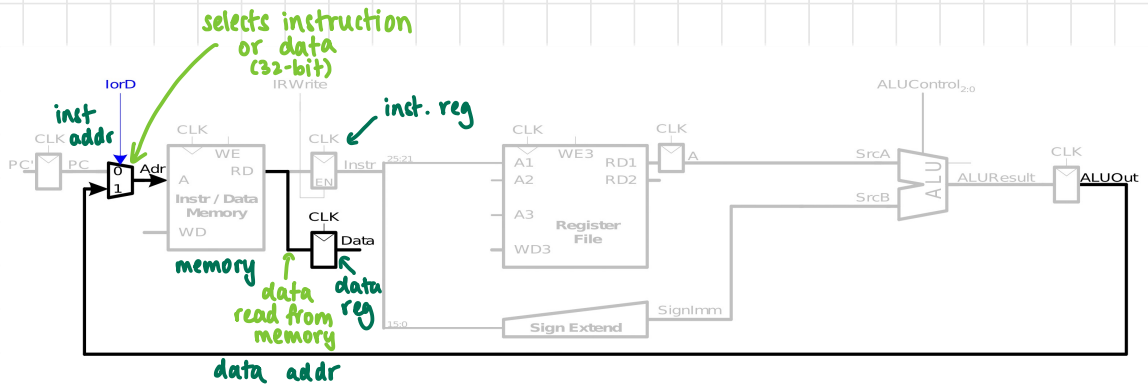

Step 5 - Write data back into RF

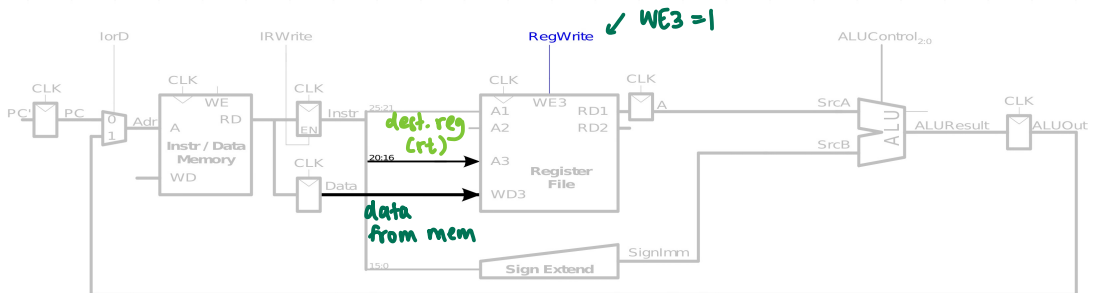


Recall: I-type instruction

OP	rs	rt	imm
6 bits	5 bits	5 bits	16 bits
31:26	25:21	20:16	15:0

Step 6 - Increment PC

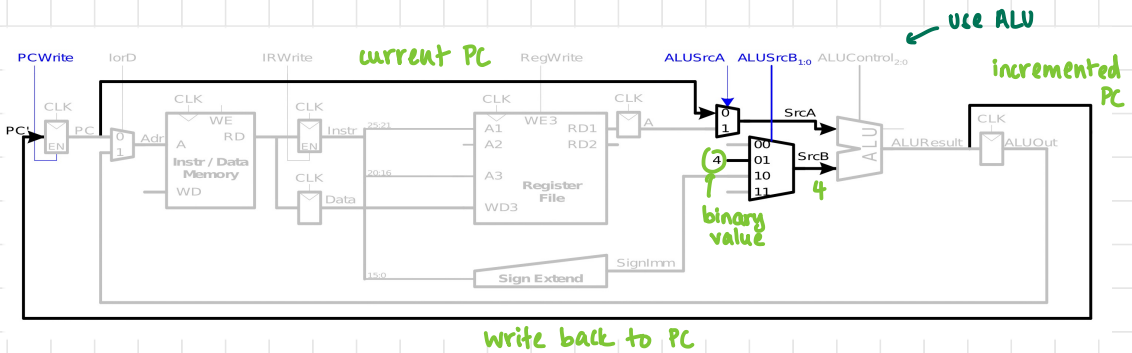- increment by 4 bytes (32-bit is 4 bytes, byte-addressable)



- Only one adder (inside ALU)
- In lab datapath design, two adders used (separate adder for PC)
- Would using two adders in current design help? How?
- Note that in both cases, architecture remains the same

Other Instructions


- sw
- R-type cadd, sub, and, ...)
- beq

Store Word Instruction

sw \$s0, 7(\$0) # write the value in \$s0 to loc 7
 rt rs

- Address computation same as for lw
- Register contents to be written to main memory
- Steps 1, 2 and 3 same as in lw
- Step 4: Register contents to be written into computed memory address

Write to Memory

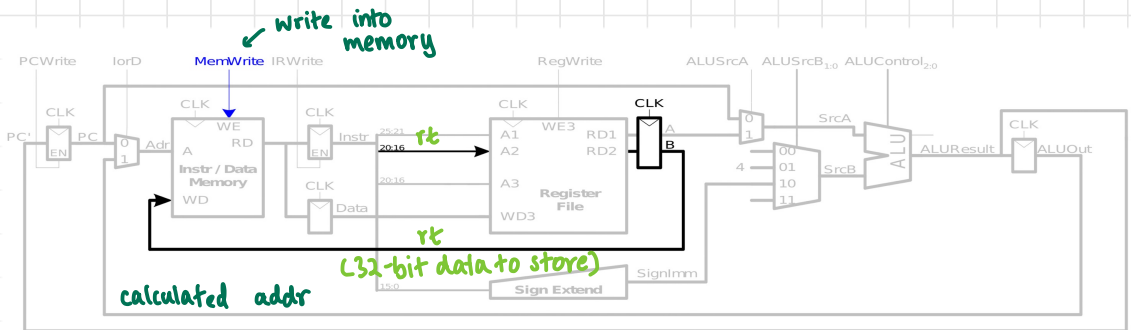


Recall: I-type instruction

OP	rs	rt	imm
6 bits	5 bits	5 bits	16 bits
31:26	25:21	20:16	15:0

R-type Instructions

- Step 1 (fetch): same as lw
 - Step 2: similar to lw (no sign extending; read 2 operands)
 - Step 3: write ALU output into destination register
-
- Read from rs and rt
 - Write ALU Result to reg file
 - Write to rd (instead of rt)

add \$s0, \$s1, \$s2
 rd rs rt

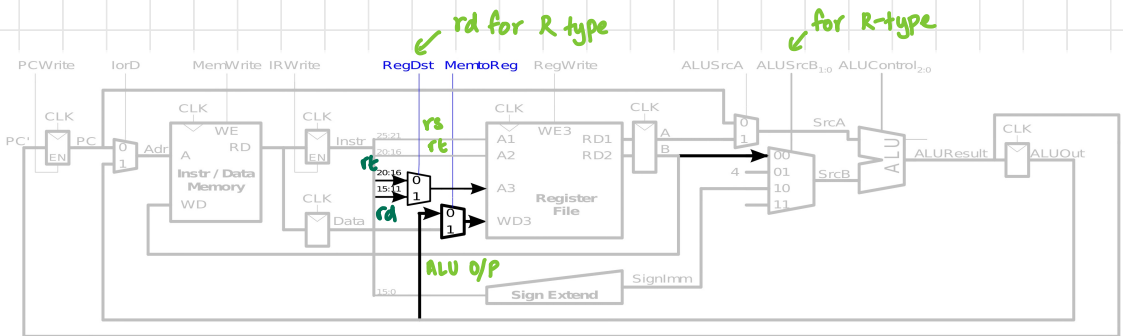

Recall: R-type instruction


OP	rs	rt	rd	shamt	funct
6 bits	5 bits	5 bits	5 bits	5 bits	6 bits
31:26	25:21	20:16	15:11	10:6	5:0

beq Instruction

- Step 1: fetch
- Step 2: compare register contents
- Step 3: change PC contents (if registers equal)

beq \$s0, \$s1, loop (PC relative)

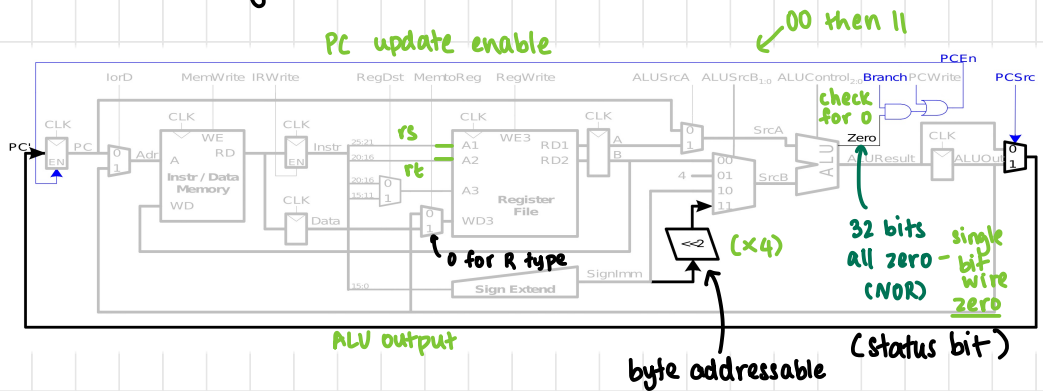rs == rt? offset value $\times 4$ ($\ll 2$) next PC inst
 BTA = (sign-extended immediate $\ll 2$) + (PC + 4)



Recall: I-type instruction

OP	rs	rt	imm
6 bits	5 bits	5 bits	16 bits
31:26	25:21	20:16	15:0